

Computer Arithmetic

Readings: 3.1-3.3, A.5

Review binary numbers, 2's complement

Develop Arithmetic Logic Units (ALUs) to perform CPU functions.

Introduce shifters, multipliers, etc.

Binary Numbers

Decimal: $469 = 4 \cdot 10^2 + 6 \cdot 10^1 + 9 \cdot 10^0$

Binary: $01101 = 1 \cdot 2^3 + 1 \cdot 2^2 + 0 \cdot 2^1 + 1 \cdot 2^0 = (13)_{10}$

Example: $0111010101 = (?)_{10}$

2's Complement Numbers

Positive numbers & zero have leading 0, negative have leading 1

Negation: Flip all bits and add 1

Ex: $-(01101)_2 =$

To interpret numbers, convert to positive version, then convert:

11010 =

01100 =

Sign Extension

Conversion of n-bit to (n+m)-bit 2's complement: replicate the sign bit

$$b_3b_2b_1b_0 = b_3b_3b_3b_2b_1b_0 = b_3b_3b_3b_3b_3b_3b_3b_3b_3b_3b_2b_1b_0$$

Ex - Convert to 8-bit: $01101 = (13)_{10}$

$11101 = (-3)_{10}$

Arithmetic Operations

Decimal:

$$\begin{array}{r} 5\ 7\ 8\ 9\ 2 \\ +\ 7\ 8\ 9\ 5\ 6 \\ \hline \end{array}$$

Binary:

$$\begin{array}{r} 1\ 0\ 1\ 0\ 1\ 1\ 1 \\ +\ 0\ 1\ 0\ 0\ 1\ 0\ 1 \\ \hline \end{array}$$

Binary:

$$\begin{array}{r} 1\ 0\ 1\ 0\ 0\ 1\ 1\ 0 \\ -\ 0\ 0\ 0\ 1\ 0\ 1\ 1\ 1 \\ \hline \end{array} \quad \rightarrow \quad \begin{array}{r} 1\ 0\ 1\ 0\ 0\ 1\ 1\ 0 \\ +\ \underline{\hspace{1cm}} \\ \hline \end{array}$$

Overflows

Operations can create a number too large for the number of bits

n-bit 2's complement can hold $-2^{(n-1)} \dots 2^{(n-1)}-1$

Can detect overflow in addition when highest bit has carry-in $\neq$ carry-out

$$(\text{carry-in}) \oplus (\text{carry-out}) = 1$$

$$\begin{array}{r} 5 \\ 3 \\ \hline -8 \end{array}$$

Overflow

$$\begin{array}{r} 0101 \\ 0011 \\ \hline \end{array}$$

$$\begin{array}{r} -7 \\ -2 \\ \hline 7 \end{array}$$

Overflow

$$\begin{array}{r} 1001 \\ 1110 \\ \hline \end{array}$$

$$\begin{array}{r} 5 \\ 2 \\ \hline 7 \end{array}$$

No overflow

$$\begin{array}{r} 0101 \\ 0010 \\ \hline \end{array}$$

$$\begin{array}{r} -3 \\ -5 \\ \hline -8 \end{array}$$

No overflow

$$\begin{array}{r} 1101 \\ 1011 \\ \hline \end{array}$$


Full Adder

A	B	CI	CO	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Multi-Bit Addition

A_3 B_3 A_2 B_2 A_1 B_1 A_0 B_0

 
$$\begin{array}{r} A_3 A_2 A_1 A_0 \\ + B_3 B_2 B_1 B_0 \\ \hline \end{array}$$




S_3

 

S_2

 

S_1

 

S_0

Adder/Subtractor

$$A + B =$$

$$A - B =$$

A_3

B_3

A_2


B_2

A_1


B_1

A_0


B_0

 


S_3

 

S_2

 

S_1

 

S_0


Overflow

Debugging Complex Circuits

Complex circuits require careful debugging

Rip up and retry?

Ex. Circuit to see if $A+B>7$.

 

Debugging Complex Circuits (cont.)

```
module fullAdd (Cout, S, A, B, Cin);  
    output Cout, S; input A, B, Cin;  
  
    assign Cout = (A&B) | (A&Cin) | (B&Cin);  
    assign S = A^B^Cin;  
endmodule
```

```
module halfAdd (Cout, S, A, B);  
    output Cout, S; input A, B;  
  
    fullAdd a1(.Cout, .S, .A, .B, .Cin);  
endmodule
```

```
module greaterThan7 (Out, A, B);  
    output Out; input [2:0] A, B; wire [3:0] C, S;  
  
    halfAdd pos0(.Cout(C[0]), .S(S[0]), .A(A[0]), .B(B[0]));  
    fullAdd pos1(.Cout(C[1]), .S(S[1]), .A(A[1]), .B(B[1]), .C(C[0]));  
    fullAdd pos2(.Cout(C[2]), .S(S[2]), .A(A[2]), .B(B[2]), .C(C[1]));  
    fullAdd pos3(.Cout(C[3]), .S(Out), .A(A[3]), .B(B[3]), .C(C[2]));  
endmodule
```

Debugging Approach

Test all behaviors.

All combinations of inputs for small circuits, subcircuits.

Identify any incorrect behaviors.

Examine inputs and outputs to find earliest place where value is wrong.

Typically, trace backwards from bad outputs, forward from inputs.

Look at values at intermediate points in circuit.

DO NOT RIP UP, DEBUG!


ALU: Arithmetic Logic Unit

Computes arithmetic & logic functions based on controls

Add, subtract

XOR, AND, NAND, OR, NOR

==, <, overflow, ...

 


Bit Slice ALU Design

Add, Subtract, AND, OR

A_i _____


B_i _____

 

Bit Slice ALU Design (cont.)

Route Carries

Overflow, zero, negative

 

Shifter

Support shift operations: $(A \ll 001101)$

Optional shift by one: $(A \ll b_0)$

Optional shift by two: $(A \ll b_1)$

Shifter (cont.)

Multiplication

Example

Multiplicand:	0	1	1	0	6
Multiplier:	0	1	0	1	5

4 partial products

30

Repeat n times:

Compute partial product; shift; add

NOTE: Each bit of partial products is just an AND operation

Parallel Multipliers

